

Matthew Borger, A08781527

Jennifer Delizo, A94013393

Clarence Lam, A08676105

Arthur Robertson, A08280000

100/100
Sahar


98
/ 100

ECE 108 Homework 2

 1) CMOS Inverter Design and Characterization

$$k_p = k_n = k' \left(\frac{W}{L} \right)$$
$$9 \times 10^{-5} \left(\frac{W_n}{L_n} \right) = 2.20 \times 10^{-5} \left(\frac{W_p}{L_p} \right)$$
$$\frac{9 \times 10^{-5}}{2.20 \times 10^{-5}} 1 \times 10^{-6} = W_p \rightarrow W_p = 4.09 \mu\text{m}$$

According to our SPICE simulation, our gate width is $4.7 \mu\text{m}$. The difference in the width can be attributed to the assumptions made in our calculations. In order for a CMOS inverter to be symmetric, the voltage thresholds should be equal. However, if we look at the SPICE model of the NMOS and PMOS transistors, we observe that the V_T 's are slightly off.




From SPICE, we obtained the output voltages:

For $V_{in} = 1.4V$, $V_{out} = 2.7335V$.

For $V_{in} = 1.5V$, $V_{out} = 1.5V$.

 For $V_{in} = 1.6V$, $V_{out} = 0.366063V$.



Below are the calculations for output voltage:

for $V = 1.4V$

$$V_{out} = V_{in} - V_{TL} + \sqrt{(V_{in} - V_{DD} - V_{TL})^2 - \frac{1}{B}(V_{in} - V_{DD})^2}$$

$$= 1.4 - 0.74 + \sqrt{(1.4 - 3 - .74)^2 - \frac{1}{4.4}(1.4 - 3)^2}$$

$$V_{out} = 2.46V$$

for $= 1.5V$

$V_{out} = 1.5V$ by definition of symmetric inverter

for $V = 1.6V$

$$V_{out} = V_{in} - V_{TD} - \sqrt{(V_{in} - V_{TD}) - (V_{in} - V_{TD})^2}$$

$$= 1.6 - 0.74 - \sqrt{(1.6 - .74) - (1.6 - .74)^2}$$

$$V_{out} = 0.513V$$

As expected, our output voltage for $V_{in} = 1.5V$ is $1.5V$. That's because we designed our CMOS inverter to have symmetric characteristics and by definition, $V_{in} = V_{DD}/2$. For $V_{in} = 1.4V$, we

simulated $V_{out} = 2.7335V$ and we calculated $V_{out} = 2.46V$. For $V_{in} = 1.6V$, we calculated $V_{out} = 0.513V$ and we simulated $V_{out} = 0.366063V$. These slight differences can be attributed to the assumptions made in our calculations and that we used approximated equations to calculate our result.

Our static noise margins for the symmetric CMOS inverter are $NM_L = 1.12$ and $NM_H = 1.05$.



Below are the calculations for the rise and fall times and the propagation delay for 100fF and 1pF:

$$C = 100fF$$

$$t_r = \frac{3CV_{DD}^2}{k_L(V_{DD} - V_{TL})^2(2V_{DD} - V_{TL})}$$

$$= \frac{3 * 100 * 10^{-15} * 9}{2.2 * 10^{-5} \left(\frac{4.09 * 10^{-6}}{1 * 10^{-6}} \right) (3 - 0.73886)^2 (2 * 3 - 0.73886)}$$

$$= 1.12ns$$

$$C = 100fF$$

$$t_f = \frac{3CV_{DD}^2}{k_D(V_{DD} - V_{TD})^2(2V_{DD} - V_{TD})}$$

$$= \frac{3 * 100 * 10^{-15} * 9}{9 * 10^{-5} \left(\frac{1 * 10^{-6}}{1 * 10^{-6}} \right) (3 - 0.743469)^2 (2 * 3 - 0.743469)}$$

$$= 1.12ns$$

Propagation Delay: 1.12 ns

$$C = 1pF$$

$$t_r = \frac{3CV_{DD}^2}{k_L(V_{DD} - V_{TL})^2(2V_{DD} - V_{TL})}$$

$$= \frac{3 * 1 * 10^{-12} * 9}{2.2 * 10^{-5} \left(\frac{4.09 * 10^{-6}}{1 * 10^{-6}} \right) (3 - 0.73886)^2 (2 * 3 - 0.73886)}$$

$$= 11.2ns$$

$$C = 1pF$$

$$t_f = \frac{3CV_{DD}^2}{k_D(V_{DD} - V_{TD})^2(2V_{DD} - V_{TD})}$$

$$= \frac{3 * 1 * 10^{-12} * 9}{9 * 10^{-5} \left(\frac{4.09 * 10^{-6}}{1 * 10^{-6}} \right) (3 - 0.743469)^2 (2 * 3 - 0.743469)}$$

$$= 11.2ns$$


Propagation Delay: 11.2 ns

Below is a table with the rise and fall times, as well as the propagation delays, for our SPICE simulations.

C	t _r	t _f	t _{pdr}	t _{pdf}	t _{pd}
C = 100fF	2.12ns	1.6646ns	1.775ns	1.2593ns	1.5172ns
C = 1pF	20.305ns	14.2356ns	16.398ns	11.357ns	13.878ns

Here are the SPICE simulations for the rise and fall times and propagation delays.

For C = 100fF

 
t_r 

 bias (active)

e step = 60.05E-12 Time = 60.00E-09 End = 60.00E-09									
X1									
Y1									
Y2									
Y1 - Y2									
Y1(Cursor1) - Y2(Cursor2)									
-1.7960									
Trace Color									
Trace Name									
Y1									
Y2									
Y1 - Y2									
Y1(Cursor1) - Y2(Cursor2)									
Max Y									
Min Y									
Avg Y									
X Values									
Y1									
Y2									
Y1 - Y2									
Y1(Cursor1) - Y2(Cursor2)									
0.000									
0.000									
2.4135									
617.516n									
1.5155									
CURSOR 12									
617.516n									
2.4135									
-1.7960									

e step = 60.05E-12 Time = 60.00E-09


End = 60.00E-09

  t_f 

 bias (active)

[illegible]

t_{pdr}

 


t_{pdr}



For C = 1pF,

t_r

 


bias (active)

step = 60.05E-12 Time = 60.00E-09 End = 60.00E-09

Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	-1.7960		
	X Values	51.746n	53.866n	-2.1200n	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y	Min Y
CURSOR 1,2	V(vout)	617.516m	2.4135	-1.7960	0.000	0.000	2.4135	617.516m

t_r

 


bias (active)


step = 60.05E-12 Time = 60.00E-09 End = 60.00E-09

Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	1.7967		
	X Values	5.5034n	19.739n	-14.235n	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y	Min Y
CURSOR 1,2	V(vout)	2.3969	600.231m	1.7967	0.000	0.000	2.3969	600.231m


t_{pdr}

 

t_{pdr}

 

 From the SPICE simulation below, our maximum input frequency is 10.638MHz.



We calculated our power dissipation to be. The following steps show how we calculated our answer:

$$P = CV_{DD}^2 f$$

$$= 1 * 10^{-12} * 9 * 10.638 \times 10^6$$

$$= 95.74 \mu W$$

Below are the transfer characteristics of our symmetric inverter after increasing the gate width of the PMOS transistor by 10X.




From SPICE, we simulated our noise margins to be $N_{ML} = 2.00$ and $N_{MH} = 0.449$. We observe that our noise margins are now worse with an asymmetric CMOS inverter. N_{MH} decreases because V_{in} must become relatively high (small range for valid V_{in} high) to overcome the large amount of current from the PMOS that fills the capacitor, while the NMOS drains current more slowly. N_{ML} increases since the strong current from the PMOS flows readily into the capacitor for a great range of V_{in} low, while CMOS characteristics guarantee sharp transition and low V_{OL} .

We simulated the rise and fall times for a load capacitance of 1pF to be $t_r = 2.547\text{ns}$ and $t_f = 14.55\text{ns}$. Since the PMOS transistor is significantly larger, it conducts much more current and is thus able to fill the capacitor much faster. Consequently, the rise time is much faster than the fall time. Therefore the clock cycle is now limited by the NMOS. The power dissipation should increase since we are sinking more current in our CMOS. Especially at transition voltage, more current will flow from V_{DD} to ground. Leakage currents will have more of an effect.




 2) CMOS NAND Gate Design and Characterization

For the worst case setup the nMOS pull-down widths should be 2um. This is because the pull-down of the NAND gate is in series. Effective length is 2um, and width must be doubled to match. For the pMOS pull-ups, the worst case is when only one of the pull-ups is on. The W/L ratios remain the same. ✓



 Transfer characteristic for $V_{IN1} = V_{IN2}$ swept from 0 to 3V. $V_{INV} = 1.58V$.



Transfer characteristic for $V_{IN1} = V_{DD}$ and V_{IN2} swept from 0 to 3V. $V_{INV} = 1.22V$.

Type up β_r equations and V_{INV} equations.

$$\beta_r = \frac{k_D' \times \left(\frac{W}{L}\right)_D}{k_L' \times \left(\frac{W}{L}\right)_D}$$

Worst case:

$$\beta r = \frac{9e^{-6} \times \frac{2}{2}}{2.2e^{-6} \times \frac{4.09}{1}}$$

$$\beta r = 1$$

$$V_{inv} = \frac{V_{dd} + V_{tL} + V_{tD}(\sqrt{\beta r})}{1 + \sqrt{\beta r}}$$

$$V_{inv} = \frac{3 - .73886 + .743469(\sqrt{2})}{1 + \sqrt{2}}$$

$$V_{inv} = 1.502V$$

Best case:

$$\beta r = 1/2$$

Since inputs are tied,

$$V_{inv} = \frac{V_{dd} + V_{tL} + V_{tD}(\sqrt{\beta r/n^2})}{1 + \sqrt{\beta r/n^2}}$$

$$V_{inv} = \frac{3 - .73886 + .743469(\sqrt{2/4})}{1 + \sqrt{2/4}}$$


$$V_{inv} = 1.865V$$


Maximum shift is .363 V

PSPICE shift is .360V


error of .826%



 


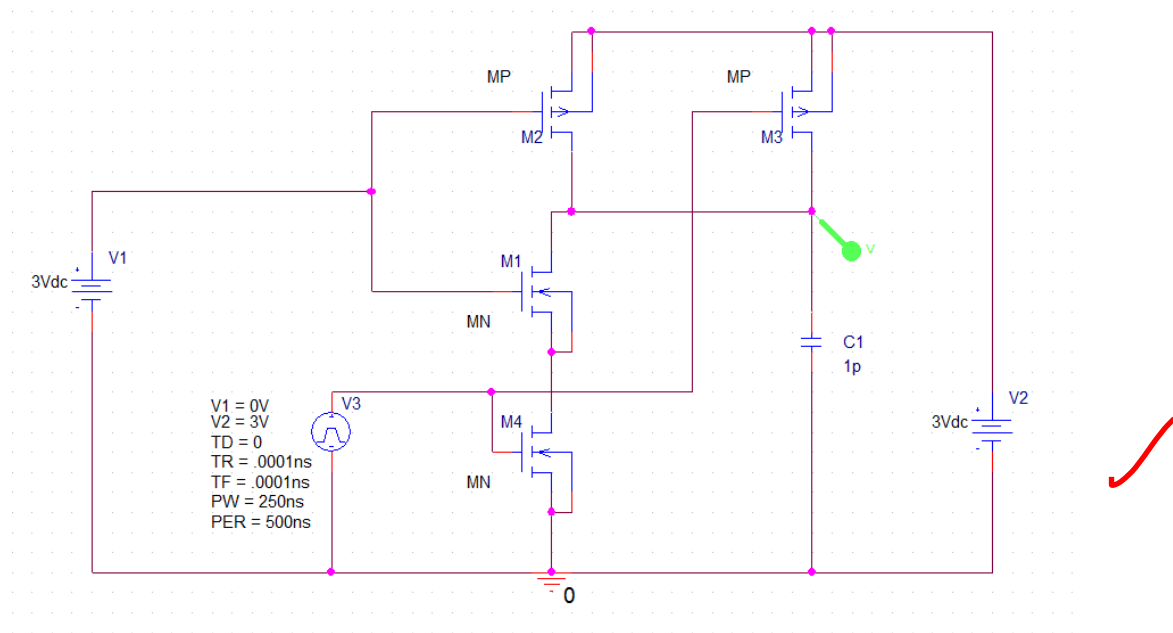


Configuration for part 2.

 

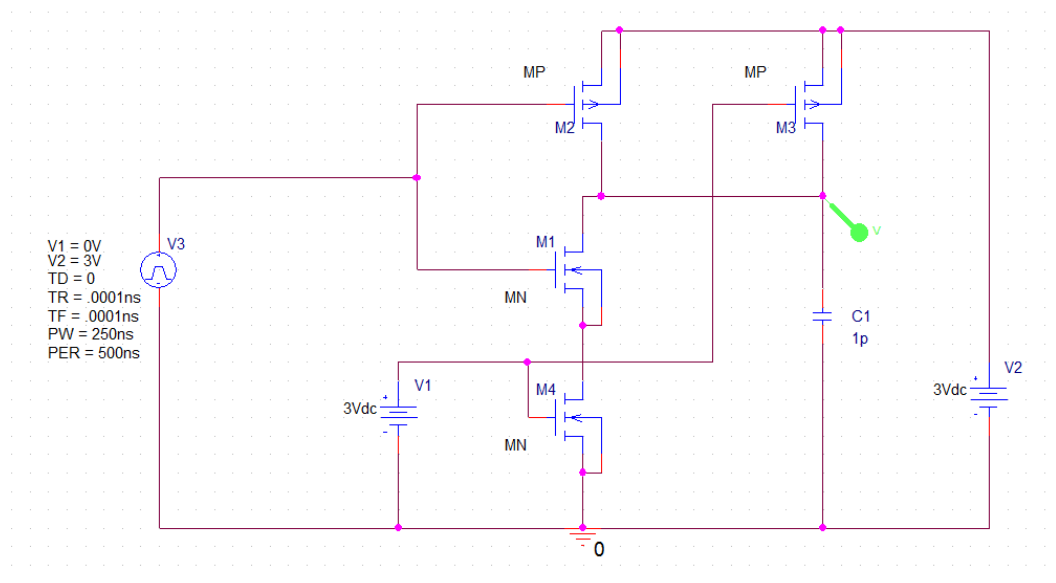VTC for part 2. $V_{INV} = 1.22V$ as seen from the cursor.



Configuration for part 3.

 

VTC for part 3. $V_{INV} = 1.27V$ as seen from the cursor.

	t_r (ns)	t_f (ns)	t_{pdr} (ns)	t_{pdf} (ns)	t_{pd} (ns)
V1 pulse, V2 high	26.684	11.090	19.497	8.191	13.844
V2 pulse, V1 high	21.404	11.800	16.554	8.165	12.360
V1, V2 tied, pulse	10.264	12.296	8.313	8.427	8.379
Inverter	20.305	14.2356	16.398	11.357	13.878

Note some discrepancy between V1 and V2 individual pulse, which is expected to be the same. This was caused by experimental error.

As expected, tied inputs have a significantly reduced rise time and rising propagation delay. This is due to the effective width of the pMOS doubling, which results in more current flow. ✓

Measurements of rise and rising propagation delay are similar for one input pulse in the NAND gate and the reference inverter. The width is doubled for the drivers in the NAND gate to counteract the doubled effective length and match the reference inverter. This results in a small boost in current at the transition point and accounts for the slight decrease in fall and falling propagation delay times.

For V1 pulse, V2 high:

t_f/t_r




t_{pd}




For V2pulse, V1 high:

t_{pd}

 


t_f/t_r

 


For V1 and V2 tied pulse

t_{pd}

 

t_f/t_r

 

Based on our findings with the NAND gate, we would expect slightly slower rise and rising propagation delay times, as the pMOS load carriers are holes. Mainly, since the nMOS are in parallel, we would expect similar performance to the reference inverter in fall and falling propagation delay times for a one input pulse. For a tied input pulse, fall and falling propagation delay times would decrease. ✓

comparing NOR gate to a
NAND gate?

3/5 5/5
Sahar